




Engineering Projects

Projects for Engineering Students

Subscribe to success,
for less.

Save on LabVIEW performance
when you subscribe.

Save now

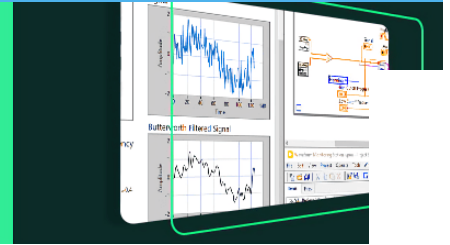

You are here ► Home > Electronics Projects > 10 Band Graphic Equalizer Circuit

10 Band Graphic Equalizer Circuit

May 31, 2021 Engineering Projects

This article is dedicated to those who want to make their high-quality low distortion 10 band graphic equalizer circuit. Before going to the circuit and it's working let's understand an equalizer and its types. An equalizer is simply a device that is attached to an instrument and with the help of this equalizer, we can set bass, middle, or treble.




Sound or audio has a spectrum where frequencies are classified into different ranges. So, what are these bass, middle and treble? These are the range of frequencies, where the bass is the lower frequency range, middle means the middle frequency range, and treble is the higher frequency range.

Different instruments have different frequency ranges. Let's for an example, in any live music

performance show where various instruments are being played by different musicians along with a vocalist if these sounds produced, were of the same frequency then the listener or audience cannot differentiate which sound is produced by which instruments. Hence, an equalizer helps in differentiating that this is the sound coming from a guitar, a tabla, a drum, or the vocalist's sound.


Talking about history, in the 1920s, the use of equalizers started in the telecommunication industry. After that, in the 1930s the first variable equalizer was invented from which many audio companies in the UK were influenced. With the advancement of technology, software started being incorporated into the music industry. The equalizer along with the hardware is now incorporated with the software. Talking about the 21st century, maximum music software or music devices have inbuilt equalizers. Now, there are several types of equalizers, some of them are, Bell, Shelving, Graphical, Semi-Parametric, and Parametric equalizers. Parametric equalizers are popular but less than graphic equalizers because graphic equalizers are more popular as these are used in our mobile phones, music players and audio/video editing which is simply used either to boost or cut the specific frequency range improving



Subscribe to
success, for less.

Save on LabVIEW performance
when you subscribe.

Save now

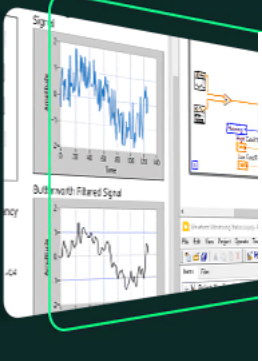

Categories

555 Timer Projects (67)

8051 Projects (12)

AC Voltage Stabilizer (6)

alarm / sound generator (33)

Amplifier Circuit (26)


Antenna Fundamental (11)



Subscribe to success, for less.

Save on LabVIEW performance when
you subscribe.

Save now

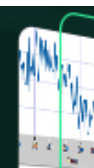

125Hz. This is done only to round up the frequency.

Table 1	
Number of bands	10 (32Hz, 64Hz, 125Hz, 250Hz, 500Hz, 1KHz, 2KHz, 4KHz, 8KHz, 16KHz)
Boost/cut on each band	±15dB
THD% (At Vout = 1V)	<0.05%
S/N Ratio	>80dB
Input impedance (Zin)	100K
Output impedance (Zout)	<150 ohms
Input voltage for Vout=1V	180mV
Max. input voltage	10V
Max. input voltage for undistorted sound	2.5V

Basic Equalizer Circuit

The circuit diagram of the basic equalizer is shown in figure 1. This circuit uses capacitors to fix the frequency as a result its roll-off is not sharp or step. This led to a lower cut and boost. This type of circuit also limits the gain or cut as a result there would be no relation betwhe een next or preceding frequency.

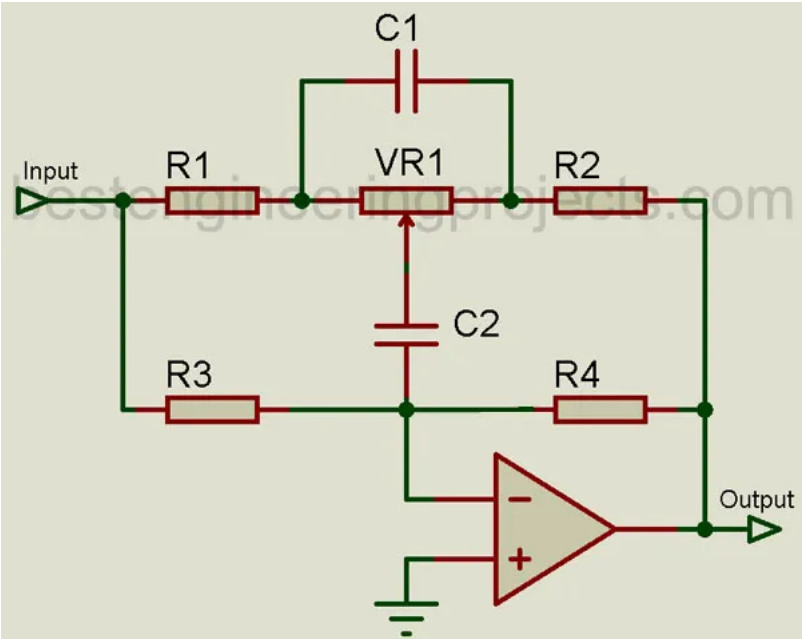


Figure 1: Normal Equaliser Circuit

Calculation for Basic Equalizer (Figure 1)

$$Boost = \frac{VR1 + R2}{R1}$$

- Basic Electronic Projects (46)
- Battery Charger Circuit (14)
- Bearing Capacity Theories (17)
- C Based Project (18)
- C++ Based Projects (5)
- Civil Projects (121)
- Cofferdams (3)
- Computer Projects (24)
- Conductor and Connection (1)
- Digital Electronics Projects (25)
- Diode (6)
- Earth Pressure and Retaining Wall (19)
- Easy Electronics Projects (22)
- Electrical Projects (9)
- Electrical Symbols (3)
- Electronic Game and Fun Projects (12)
- Electronic Measurement and Tester Circuit (32)
- Electronic Timer Circuit (10)
- Electronic Tutorial (97)
- Electronics and Communication Projects (21)
- Electronics Design (57)
- Electronics Projects (424)
- Electronics Troubleshooting (16)
- Field Effect Transistors (3)
- Geotechnical Process (7)
- IC 741 Based Projects (35)
- IOT Projects (7)
- Led Projects (8)
- Machine Foundation (11)
- Mat Foundation (5)
- Microcontroller Projects (28)
- Microprocessor Program (2)
- Microwaves (22)
- Motor Driver Circuit (11)
- Nonsinusoidal Generator (5)

Subscribe to success, for less.


Save on LabVIEW performance when you subscribe.

Save now



Save on LabVIEW performance when you subscribe.

Save now

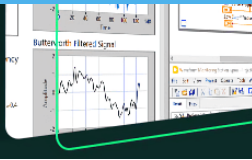

Rot

She

Site Investigation (20)

Spread Foundation (9)

ing (41)

jects (2)

22)


Circuit (16)

$$C2 = \frac{C1}{10}$$

Subscribe to success, for less.

Save on LabVIEW performance when you subscribe.

Save now

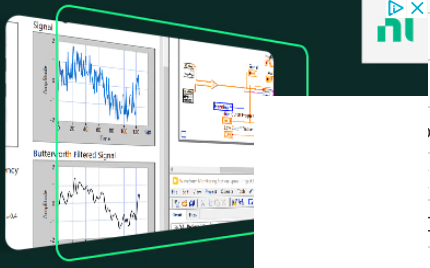

Top Posts & Pages



What are the Applications of microwaves



50+ Top 555 Timer IC Projects



Employee Management System Using C++



Top 10 Electronics Mini Projects using IC 555



Analysis of Common Emitter Amplifier using h-parameters



Common Emitter Configuration of PNP Transistor



Mini Projects using IC 741



Operation Amplifier 741 Based Projects



Amplifier Circuit Diagram



Op-amp | Block Diagram | Characteristics of Ideal and Practical Op-amp

The value of resistors R4 and R5 is usually around 1M.

Equalizer Circuit using Tuned Circuit

The equalizer circuit using a tuned circuit in the flat condition is shown in figure 2(a). This type of circuit uses a tuned circuit to fix the frequency. One can easily vary the gain and 'Q' of the equalizer as a result even designing a 30-band graphic equalizer is possible by using 2(a) circuits. In this circuit, the value of resistor R4 is very small in comparison to resistor R1, where the value of resistor R1 and R3 must be equal.

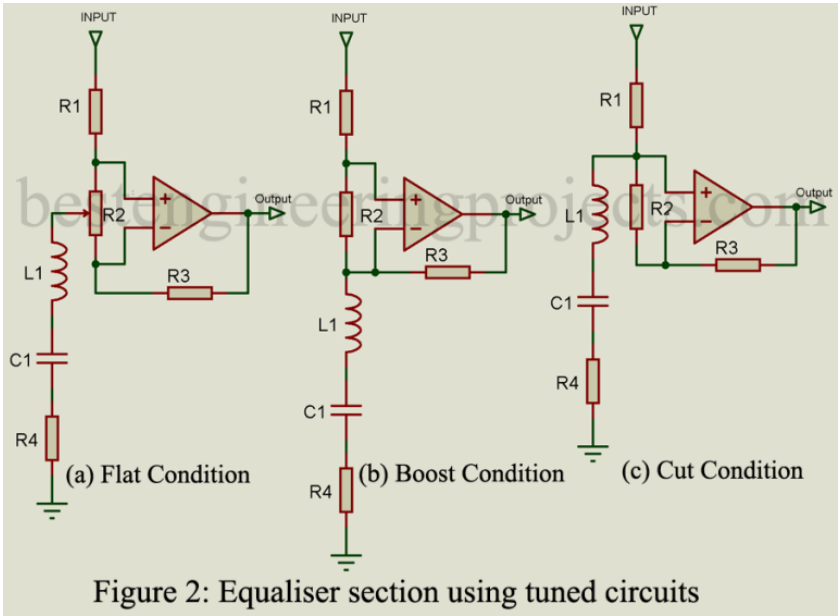


Figure 2: Equaliser section using tuned circuits




The circuit shown in figure 2(b) is in boost condition. Let us consider, the resistance of the



Subscribe to success, for less.

Save on LabVIEW performance when you subscribe.

Save now

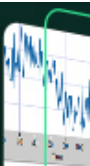




Subscribe to success,
for less.

Save on LabVIEW performance
when you subscribe.

Save now

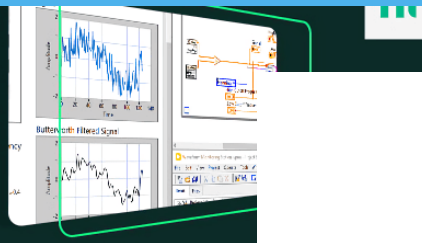


The circuit shown in figure 2(c) is in cut condition. Figure 2(a), 2(b) and 2(c) represent the same equalizer section. In figure 2(c), the input voltage is divided using two resistors R1 and R2. Some amount of input also appears at series resistor R4 because its value is very small in comparison to resistor R1. In this condition, the gain of op-amp A1 becomes zero as a result it acts as a buffer. The value of cut can be determined using relation $\frac{R4}{R4 + R1}$.

Let's consider building a 10-band graphic equalizer using the concept of the circuit shown in figure 2. At lower frequencies (say 32Hz or 64Hz) the value and size of inductor L1 become very big i.e. one inductor can occupy the entire cabinet. To solve this issue, the concept of a simulated inductor is used.

Simulated Inductor

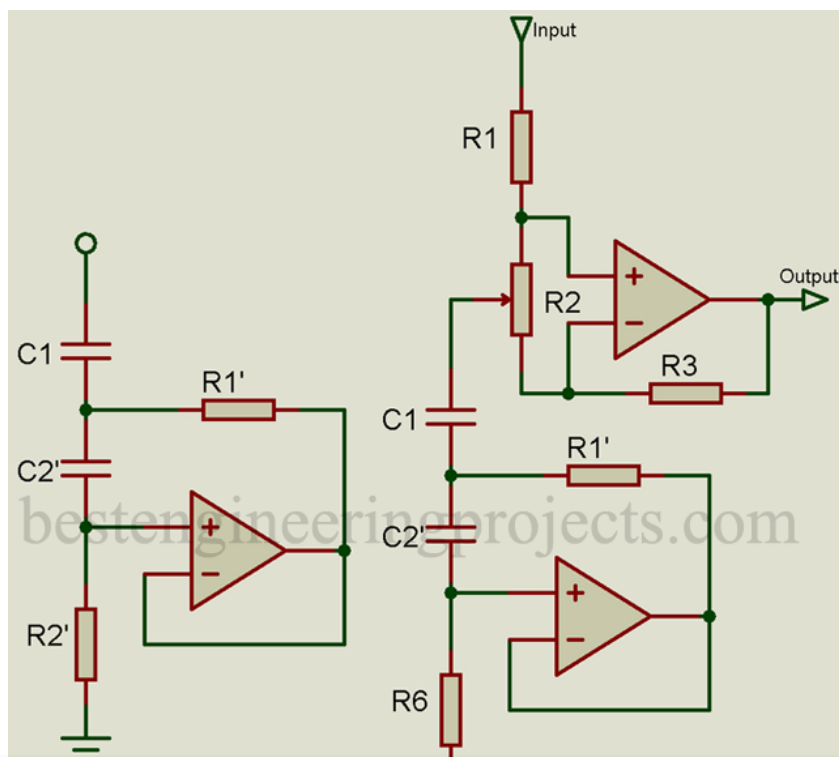
A simulated inductor is an equivalent circuit for an inductor. The basic design considering a simulated inductor is shown in figure 3(a) where figure 3(b) shows the simulated inductor incorporation in an equalizer. Capacitor C1 (figure (3a)) is the series tuning capacitor while all the other components make up the simulated inductor.



Subscribe to success, for less.

Save on LabVIEW performance when
you subscribe.


Save now

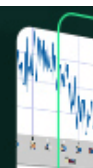



Save on LabVIEW performance
when you subscribe.

Save now

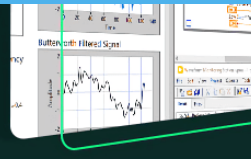

Mathematical Calculation involved in Simulator inductor

$$Q = \sqrt{\frac{C_2 R_2'}{C_1 R_1}}$$

$$f_0 = \frac{1}{2\pi \sqrt{R_1 R_2' C_1 C_2}}$$

R2 = Bias resistor for A1

R2' = Very high value like 100k or 220k

$$C_1 = \frac{1}{(2\pi f_0)^2 L}$$

$$C_2 = \frac{L}{(R_1 - R_2) R_2'}$$

$$Q = \frac{Q R_1}{2\pi f_0}$$

R1' can be calculated by first selecting R3 (In figure 3(b)) and then using the rotation

$$R_1' = \frac{R_3}{\text{BoostGain} - 1}$$

Description of 10 Band Graphic Equalizer Circuit


The circuit of the 10 band graphic equalizer is shown in figure 4. It is built around three quad op-amp IC (TL084s). The input is designed around U3:A of U3 with a gain of 5.5. Capacitor C2 acts as a very high-frequency filter. The simulated inductor is designed around ten different op-amps each for individual bands (i.e. 32Hz to 16KHz). The output is designed around op-amp U5:D. All the potentiometers (VR1 to VR10) are connected to the output op-amp U5:D. These potentiometers are used to boost or cut specified frequencies. Op-amp U5:D is a replica of A1 as shown in figure 3(b).



Subscribe to success, for less.

Save on LabVIEW performance when
you subscribe.

Save now

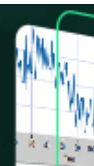

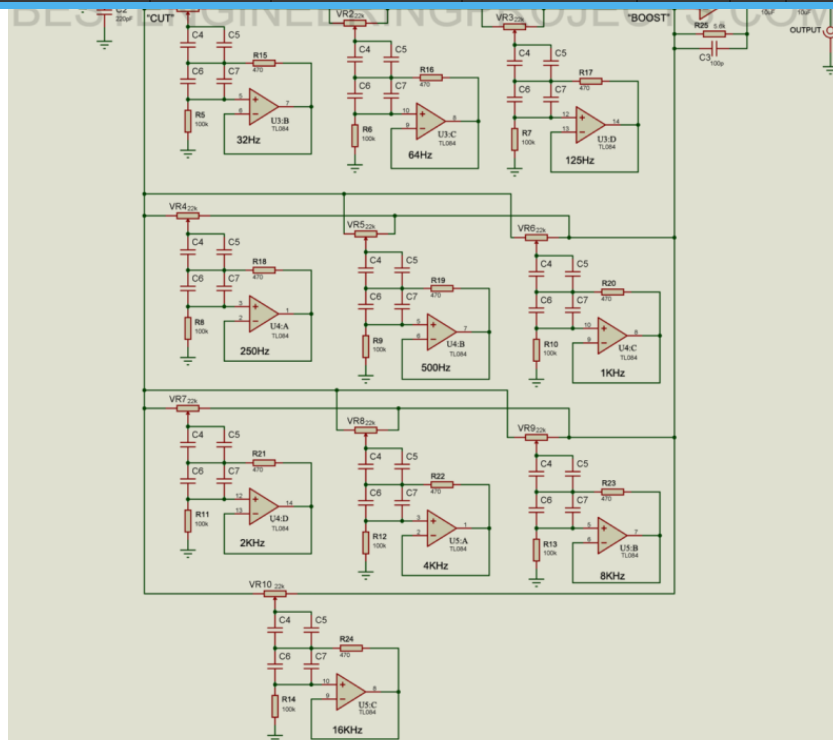


Figure 4: Circuit Diagram of a First Octave, 10-Band Graphic Equaliser

All the potentiometers used in this circuit are of logarithmic type i.e. resistance changes slowly in both the end and quickly in the middle. The reason for using this type of pot is the sensitivity of the circuit. The circuit becomes most sensitive when the value of the pot approaches 470 ohms. To solve this problem, a logarithmic potentiometer is used.


Table II				
	Values of			
Frequency	C4	C5	C6	C7
32Hz	4.7 μ F	0.56 μ F	0.1 μ F	-
64Hz	2.2 μ F	0.47 μ F	0.05 μ F	-
125Hz	1.2 μ F	0.15 μ F	0.022 μ F	2.7 kpF
250Hz	0.68 μ F	-	0.012 μ F	-
500Hz	0.33 μ F	-	6.2 kpF	-
1KHz	0.15 μ F	0.02 μ F	2.7 kpF	470 pF
2KHz	0.082 μ F	2 kpF	1.5 kpF	-
4KHz	27 kpF	15 kpF	680 pF	100 pF
8KHz	0.02 μ F	-	390 pF	-
16KHz	0.01 μ F	-	200 pF	-



Subscribe to success, for less.

Save on LabVIEW performance when you subscribe.

Save now

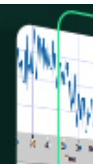



U3		
5, 6, 7	C4, C5, C6	32 Hz
8, 9, 10	C4, C5, C6	64 Hz
12, 13, 14	C4, C5, C6, C7	125 Hz
U4		
1, 2, 3	C4, C6	250 Hz
5, 6, 7	C4, C6	500 Hz
8, 9, 10	C4, C5, C6, C7	1 KHz
12, 13, 14	C4, C5, C6	2 KHz
U5		
1, 2, 3	C4, C5, C6, C7	4 KHz
5, 6, 7	C4, C6	8 KHz
8, 9, 10	C4, C6	16 KHz

The value of the capacitor is shown in table II, whereas Table III shows the number of capacitors connected to each amplifier for a different frequency. At 32Hz op-amp U3:B, only three capacitors are connected i.e. C4, C5, and C6 (Refer to table III), similarly at 64Hz only three capacitors are connected. Capacitors of polycarbonate or polyester type should be used to get a better response. Higher value capacitors say 4.7uF should be of tantalum type. To get the desired value two capacitors can be used in a back-to-back configuration. In case of nothing is available, use a high voltage electrolytic capacitor of a standard value. To achieve the correct value of the capacitor, use a capacitance meter.

Capacitors	Types
4.7μF, 2.2μF, 1.2μF	Tantalum capacitor (back to back configuration) or high voltage electrolytic capacitor (say 100V)
0.68μF, 0.47μF, 0.33μF, 0.15μF, 0.1μF, 0.082μF, 0.05μF, 0.027μF (27 kpF), 0.022μF, 0.02μF, 0.012μF, 0.01 μF, 15kpF, 6.2 kpF, 2.7 kpF, 2kpF, 1.5 kpF, 470 pF, 390 pF, 200pF	Polycarbonate (Metallized) or polyester capacitor
0.56μF, 100pF, 680μF	Ceramic Disc

Point to be Considered while designing 10 Band Graphic Equalizer Circuit

1. First, check the polarity of the power supply and connect it to the circuit
2. Then connect all the common points of the variable resistor to the non-inverting input of the output amplifier i.e. pin 12 of U5:D.
3. Before inserting IC U4, connect the power supply and check whether any other IC is heating or not.


4. Now connect the output of each amplifier and also connect these outputs to the input



Subscribe to success, for less.

Save on LabVIEW performance when you subscribe.

Save now

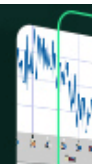

equalizer as a result these IC will get slightly hot.

Power Supply Circuit

The power supply required for this circuit is +15V and -15V, this can be achieved by using a fixed voltage regulator IC. 220V/50Hz or 110V/60Hz is given to the primary side of transformer X1 through a DPDT switch as shown in the circuit of the power supply. The secondary side is connected to a bridge rectifier built using four rectifier diodes. Pulsating DC is filtered using a capacitor network built using capacitors C16 to C19. This filtered output is further given to the fixed voltage regulator IC. The output +15V and -15V is further passed through the capacitor network built using capacitor C20 to C23. While selecting a capacitor for the power supply, try to use a polyester capacitor for 0.22μF capacitors (i.e. C18 to C21). The power supply is given to the IC through the RC network as shown in the circuit of the power supply. This is done to decouple the power supply from the IC.

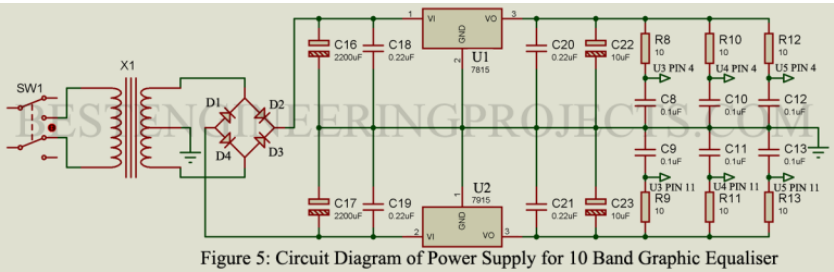


Figure 5: Circuit Diagram of Power Supply for 10 Band Graphic Equaliser

Component used in 10 Band Graphic Equalizer Circuit

Resistor (all ¼-watt, ± 5% Carbon)
R1, R3 = 100KΩ
R2 = 22KΩ
R4 = 5.6KΩ
R5 – R14 = 100KΩ
R15 – R24 = 470Ω
R25 = 5.6KΩ
VR1 – VR10 = 22KΩ Log. potentiometer
Capacitors
C1, C18-C21 = 0.22μF (Polyester Capacitor)
C2, C3 = 220pF (Styroflex Capacitor)
C4-C7 = refer Table II
C8 – C13 = 0.1 μF (Ceramic Disc Capacitor)
C14, C15, C22, C23 = 10μF/25V (Electrolytic Capacitor)
C16, C17 = 2200μF/35V (Electrolytic Capacitor)

Subscribe to success, for less.

Save on LabVIEW performance when you subscribe.

[Save now](#)



Miscellaneous

X1 = 18V-0-18V, 250mA secondary transformer

SW1 = DPDT toggle switch

Knobs for variable resistor

Shielded wire

Check out other top popular Articles :

[What is underpinning](#)

[Clock Signal Generator Circuit](#)

[Battery Voltage State Indicator](#)

[Transformer Coupled Audio Power](#)

Amplifier Circuit Electronics Projects

« Radar Waveform and Range Determination

Microwave Integrated Circuits »

LEAVE A COMMENT





Subscribe to success, for less.

Save on LabVIEW performance when you subscribe.

Save now



Name

Email

Website URL


☐ Notify me of follow-up comments by email.

☐ Notify me of new posts by email.

ADD COMMENT

Recent Posts

- Automatic Solder Smoke Extractor
- The Importance of Maintaining Elevators in Residential Units
- Arduino Countdown Timer using P10 Display
- Pulse Amplitude Modulation
- Different Ways Of Joining Metals Without Welding



Subscribe to success, for less.

Save on LabVIEW performance when you subscribe.

Save now

